

16. Esercizi dal libro vari

mercoledì 6 maggio 2020

13:30

$$(x \downarrow y) \uparrow \bar{z}$$

$$(x + y) + z$$

La freccia in basso è il NOR ($\equiv \overline{OR}$)
La freccia in alto è il NAND ($\equiv \overline{AND}$)

x	y	z	$(x \downarrow y) \uparrow \bar{z}$	$(x + y) + z$
0	0	0	$1 \uparrow 1 = 0$	$0 + 0 = 0$
0	0	1	$1 \uparrow 0 = 1$	$0 + 1 = 1$
0	1	0	$0 \uparrow 1 = 1$	$1 + 0 = 1$
0	1	1	$0 \uparrow 0 = 1$	$1 + 1 = 1$
1	0	0	$0 \uparrow 1 = 1$	$1 + 0 = 1$
1	0	1	$0 \uparrow 0 = 1$	$1 + 1 = 1$
1	1	0	$0 \uparrow 1 = 1$	$1 + 0 = 1$
1	1	1	$0 \uparrow 0 = 1$	$1 + 1 = 1$


Le due funzioni sono equivalenti. La seconda è uguale alla prima se si applica De Morgan:

$$\begin{aligned}(x + y) + z &= \overline{\overline{(x + y) + z}} = \overline{\overline{(x + y)} \cdot \bar{z}} = \\ &\quad \underline{\overline{x + y}} \equiv x \downarrow y \\ &= \overline{\underline{(x \downarrow y)} \cdot \bar{z}} = (x \downarrow y) \uparrow \bar{z} \\ &\quad \underline{a \cdot \bar{z}} \equiv a \uparrow \bar{z}\end{aligned}$$

Il circuito sequenziale riconosce la sequenza 1101 ed ha in uscita 0

es.

$t(x)$	0	1	2	3	4	5	6	...
x	0	1	1	1	0	1	0	
z	0	0	0	0	0	1	0	

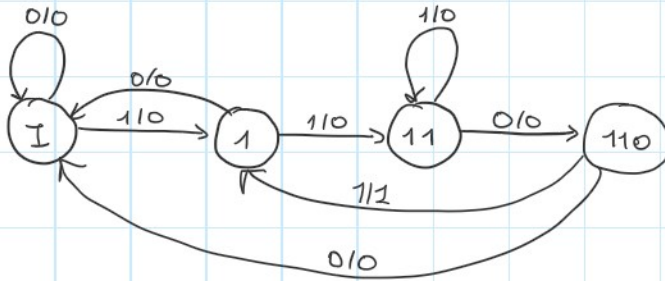

Codifica!


$$\lceil \log_2 4 \rceil = 2$$

Stato	Codifica
I	00
1	01
11	10
110	11


Tabella delle Transizioni!

		$x=0$			$x=1$		
	$y_1 y_0$	y_1'	y_0'	z	y_1'	y_0'	z
I	00	0	0	0	0	1	0
1	01	0	0	0	1	0	0
11	10	1	1	0	1	0	0
110	11	0	0	0	0	1	1

Mappe di Karnaugh!

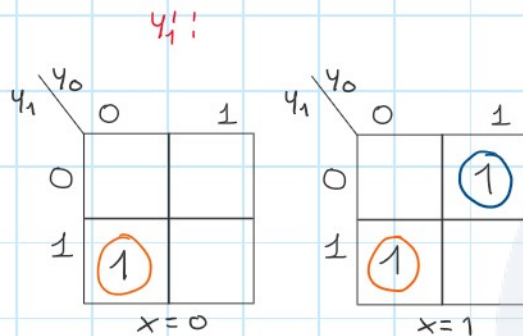
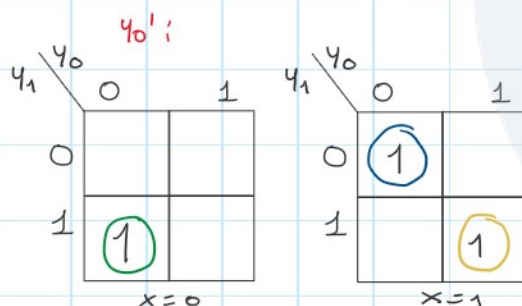
$$y_1' = y_1 \bar{y}_0 + \bar{y}_1 y_0 x$$



$$\begin{array}{|c|c|} \hline 1 & \boxed{1} \\ \hline \end{array} \quad x=0 \qquad \begin{array}{|c|c|} \hline & \boxed{1} \\ \hline \end{array} \quad x=1$$

$$y_0' = y_1 \bar{y}_0 \bar{x} + \bar{y}_1 \bar{y}_0 x + y_1 y_0 x$$

2:

$$\begin{array}{c}
 \begin{array}{cc} y_1 \backslash y_0 & 0 & 1 \\ 0 & & \\ 1 & & \end{array} \quad x=0 \qquad \begin{array}{cc} y_1 \backslash y_0 & 0 & 1 \\ 0 & & \\ 1 & & \boxed{1} \end{array} \quad x=1
 \end{array}$$

$$z = y_1 y_0 x$$